

Mess Entry Counter System Using Up/Down Counter



Indian Institute of Technology
Hyderabad

Lab Assignment : 08

EE1200: Electrical Circuits Lab

Harshil Rathan Y
Y Akhilesh

EE24BTECH11064
EE24BTECH11066

भारतीय प्रौद्योगिकी संस्थान हैदराबाद
Indian Institute of Technology Hyderabad

Contents

| | | |
|----------|---|-----------|
| 1 | Experiment Objective | 2 |
| 2 | Components Used | 2 |
| 2.1 | 7411 IC | 2 |
| 2.2 | 7432 IC | 3 |
| 2.3 | 7476 IC | 3 |
| 2.4 | 7447 IC | 4 |
| 2.5 | 7segment Display | 4 |
| 3 | Mod-10 Synchronous Up Counter | 4 |
| 3.1 | State Diagram | 5 |
| 3.2 | State Table | 5 |
| 3.3 | Expression for T_A, T_B, T_C, T_D | 6 |
| 3.3.1 | K-Map for T_A | 6 |
| 3.3.2 | K-Map for T_B | 6 |
| 3.3.3 | K-Map for T_C | 7 |
| 3.3.4 | K-Map for T_D | 7 |
| 3.4 | Circuit Diagram | 8 |
| 4 | Mod-10 Synchronous Down Counter | 8 |
| 4.1 | State Diagram | 9 |
| 4.2 | State table | 9 |
| 4.3 | Expression for T_A, T_B, T_C, T_D | 10 |
| 4.3.1 | K-Map for T_A | 10 |
| 4.3.2 | K-Map for T_B | 10 |
| 4.3.3 | K-Map for T_C | 11 |
| 4.3.4 | K-Map for T_D | 11 |
| 4.4 | Circuit diagram | 12 |
| 5 | Connections | 13 |
| 5.1 | One's Digit Up Down Counter | 13 |
| 5.2 | Ten's Digit Up Down Counter | 15 |
| 5.3 | Working 0-99-0 Up Down Counter | 16 |
| 5.4 | Complete Circuit Diagram | 17 |
| 6 | CLK Signal Generation | 17 |
| 7 | Problems Faced - Hardware | 19 |


1 Experiment Objective

To design and implement a **digital up/down counter** that displays the number of people currently in the mess during peak lunch hours. The system will help students decide whether they can enter the mess based on the current occupancy. The maximum count is set to **99**.

2 Components Used


- 1) Arduino Uno
- 2) 2 Seven-Segment Displays
- 3) 2 Push Buttons
- 4) 4 7476 JK Flip-Flop
- 5) 11 7411 AND Gate IC's
- 6) 6 7432 OR Gate IC's
- 7) 2 **7447** BCD to 7-Segment Decoder IC's
- 8) Breadboard & Jumper Wires
- 9) 2 Resistors - 220 Ω
- 10) 2 LEDs

2.1 7411 IC

 


- 7411 Triple 3-Input AND Gate IC .
- We set one input to high when we need only 2 input and gate.
- Used to build multiplication logic

2.2 7432 IC

 

- 7432 Quad 2-Input OR Gate IC .
- It has four independent gates as given in the diagram.
- Used to build addition logic

2.3 7476 IC

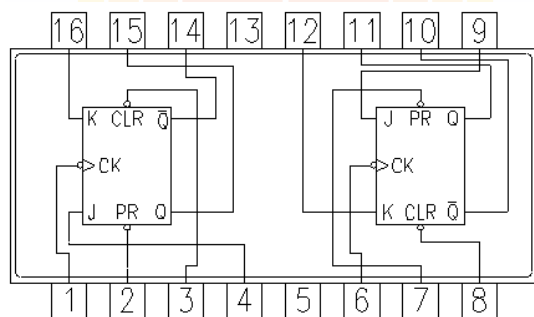

7476

Dual J/K M/S Flip-Flop
with Preset and Clear


- 7476 Dual JK FLip Flop IC's
- Each IC has 2 independent JK Flip Flops
- Used to build increment and decrement logic based on state diagram
- For this exp we used 4 independent JK Flip flops

2.4 7447 IC



- This is a BCD decoder for a 7 segment display
- It has 4 inputs A B C and D
- Connected those inputs to Q_A, Q_B, Q_C, Q_D in each condition for a displays
- It controls the outputs accordingly

2.5 7segment Display

 

- It takes inputs a, b, c, d, e, f, g and display the digit accordingly
- it can show numbers 0-9, we used 2 such displays


भारतीय प्रौद्योगिकी संस्थान हैदराबाद

3 Mod-10 Synchronous Up Counter

Indian Institute of Technology Hyderabad

- No of states count by counter = $N = 10$.
- Range of counting = 0 to $N-1 = 0$ to 9.
- Number of Flip Flops = 2 IC's

3.1 State Diagram

 

3.2 State Table

| State | Present State | | | | Next State | | | | Inputs (T Flip-Flops) | | | |
|-------|---------------|-------|-------|-------|------------|-----------|-----------|-----------|-----------------------|-------|-------|-------|
| | Q_A | Q_B | Q_C | Q_D | Q_{A+1} | Q_{B+1} | Q_{C+1} | Q_{D+1} | T_A | T_B | T_C | T_D |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 2 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 5 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 6 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 9 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 | x | x | x | x | x | x | x | x |
| 11 | 1 | 0 | 1 | 1 | x | x | x | x | x | x | x | x |
| 12 | 1 | 1 | 0 | 0 | x | x | x | x | x | x | x | x |
| 13 | 1 | 1 | 0 | 1 | x | x | x | x | x | x | x | x |
| 14 | 1 | 1 | 1 | 0 | x | x | x | x | x | x | x | x |
| 15 | 1 | 1 | 1 | 1 | x | x | x | x | x | x | x | x |

- Since the 7 segment display displays 0-9 we ignore states from 10-15
- States from 10 to 15 are of **Don't care conditions**

3.3 Expression for T_A , T_B , T_C , T_D

$$T_A = \sum m(7, 9) + d(10, 11, 12, 13, 14, 15)$$

$$T_B = \sum m(3, 7) + d(10, 11, 12, 13, 14, 15)$$

$$T_C = \sum m(1, 2, 5, 7) + d(10, 11, 12, 13, 14, 15)$$

$$T_D = \sum m(0, 1, 2, 3, 4, 5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

3.3.1 K-Map for T_A

| | | $Q_C Q_D$ | | | |
|-----------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| $Q_A Q_B$ | 00 | 0 | 0 | 0 | 0 |
| | 01 | 0 | 0 | 1 | 0 |
| | 11 | x | x | x | x |
| | 10 | 0 | 1 | x | x |

$$T_A = Q_A \cdot Q_D + Q_B \cdot Q_C \cdot Q_D$$

3.3.2 K-Map for T_B

| | | $Q_C Q_D$ | | | |
|-----------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| $Q_A Q_B$ | 00 | 0 | 0 | 1 | 0 |
| | 01 | 0 | 0 | 1 | 0 |
| | 11 | x | x | x | x |
| | 10 | 0 | 0 | x | x |

$$T_B = Q_C \cdot Q_D$$

3.3.3 K-Map for T_C

| | | $Q_C Q_D$ | | | |
|-----------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| $Q_A Q_B$ | 00 | 0 | 1 | 1 | 0 |
| | 01 | 0 | 1 | 1 | 0 |
| | 11 | x | x | x | x |
| | 10 | 0 | 0 | x | x |


$$T_C = \overline{Q_A} \cdot Q_D$$

3.3.4 K-Map for T_D

| $Q_C Q_D$ | | $Q_A Q_B$ | | | |
|-----------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| $Q_A Q_B$ | 00 | 1 | 1 | 1 | 1 |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | x | x | x | x |
| | 10 | 1 | 1 | x | x |

$$T_D = 1$$

3.4 Circuit Diagram

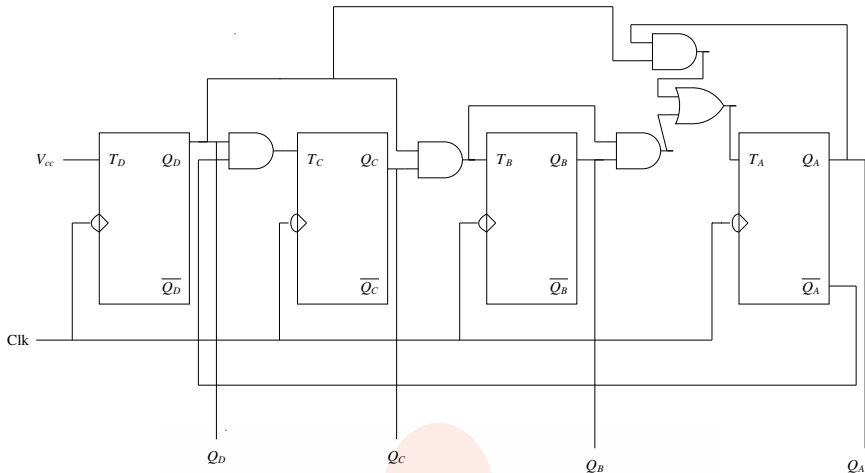

Circuit Logic Summary

-
-
-
-

$$T_D = 1$$

$$T_C = \overline{Q_A} \cdot Q_D$$

$$T_B = Q_C \cdot Q_D$$


$$T_A = Q_A \cdot Q_D + Q_B \cdot Q_C \cdot Q_D$$

Implement and connect the following logics according to the circuit diagram above with the help of the gates

4 Mod-10 Synchronous Down Counter

- No of states count by counter = $N = 10$.
- Range of counting = $N-1$ to $0 = 9$ to 0 .
- Required Flip Flops = 2 IC's

4.1 State Diagram

 

4.2 State table

| State | Present State | | | | Next State | | | | Inputs (T Flip-Flops) | | | |
|-------|---------------|-------|-------|-------|------------|-----------|-----------|-----------|-----------------------|-------|-------|-------|
| | Q_A | Q_B | Q_C | Q_D | Q_{A+1} | Q_{B+1} | Q_{C+1} | Q_{D+1} | T_A | T_B | T_C | T_D |
| 9 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 8 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 3 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 | x | x | x | x | x | x | x | x |
| 11 | 1 | 0 | 1 | 1 | x | x | x | x | x | x | x | x |
| 12 | 1 | 1 | 0 | 0 | x | x | x | x | x | x | x | x |
| 13 | 1 | 1 | 0 | 1 | x | x | x | x | x | x | x | x |
| 14 | 1 | 1 | 1 | 0 | x | x | x | x | x | x | x | x |
| 15 | 1 | 1 | 1 | 1 | x | x | x | x | x | x | x | x |

4.3 Expression for T_A , T_B , T_C , T_D

$$T_A = \sum m(0, 8) + d(10, 11, 12, 13, 14, 15)$$

$$T_B = \sum m(4, 8) + d(10, 11, 12, 13, 14, 15)$$

$$T_C = \sum m(0, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$$

$$T_D = \sum m(0, 1, 2, 3, 4, 5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

4.3.1 K-Map for T_A

| | | $Q_C Q_D$ | | | |
|-----------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| $Q_A Q_B$ | 00 | 1 | 0 | 0 | 0 |
| | 01 | 0 | 0 | 0 | 0 |
| | 11 | x | x | x | x |
| | 10 | 1 | 0 | x | x |

$$T_A = \overline{Q_B} \cdot \overline{Q_A} \cdot \overline{Q_D}$$

4.3.2 K-Map for T_B

| | | $Q_C Q_D$ | | | |
|-----------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| $Q_A Q_B$ | 00 | 0 | 0 | 0 | 0 |
| | 01 | 1 | 0 | 0 | 0 |
| | 11 | x | x | x | x |
| | 10 | 1 | 0 | x | x |

$$T_B = (Q_A + Q_B) \cdot \overline{Q_C} \cdot \overline{Q_D}$$

4.3.3 K-Map for T_C

| | | $Q_C Q_D$ | | | |
|-----------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| $Q_A Q_B$ | 00 | 0 | 0 | 0 | 1 |
| | 01 | 1 | 0 | 0 | 1 |
| | 11 | x | x | x | x |
| | 10 | 1 | 0 | x | x |



$$T_C = Q_C \cdot \overline{Q_D} + T_B$$

4.3.4 K-Map for T_D

| | | $Q_C Q_D$ | | | |
|-----------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| $Q_A Q_B$ | 00 | 1 | 1 | 1 | 1 |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | x | x | x | x |
| | 10 | 1 | 1 | x | x |

$$T_D = 1$$

4.4 Circuit diagram

  

where,

$$D_1 = Q_B \overline{Q_C} \cdot \overline{Q_D} + Q_A \overline{Q_C} \cdot \overline{Q_D} + Q_C \overline{Q_D}$$

$$D_2 = Q_B \overline{Q_C} \cdot \overline{Q_D} + Q_A \overline{Q_C} \cdot \overline{Q_D}$$

$$D_3 = \overline{Q_B} \cdot \overline{Q_C} \cdot \overline{Q_D}$$

$$U_1 = \overline{Q_A} Q_D$$

$$U_2 = Q_C Q_D$$

$$U_3 = Q_A \overline{Q_B} \cdot \overline{Q_C} Q_D$$

$$DE = \overline{Q_A} \cdot \overline{Q_B} \cdot \overline{Q_C} \cdot \overline{Q_D}$$

$$U_3 = Q_A Q_D + Q_B Q_C Q_D$$

$$U \rightarrow U_p$$

$$D \rightarrow \text{Down}$$

Circuit Logic Summary

-

$$T_D = 1$$

-

$$T_C = Q_C \cdot \overline{Q_D} + T_B$$

-

$$T_B = (Q_A + Q_B) \cdot \overline{Q_C} \cdot \overline{Q_D}$$

-

$$T_A = \overline{Q_B} \cdot \overline{Q_A} \cdot \overline{Q_D}$$

Implement and connect the following logics according to the circuit diagram above with the help of the gates

5 Connections

Follow the following connections


- **Step : 1**

First Make a single digit up/down counter by cascading the up and down counter which counts from 0-9 and 9-0 when buttons are pressed accordingly

Indian Institute of Technology Hyderabad

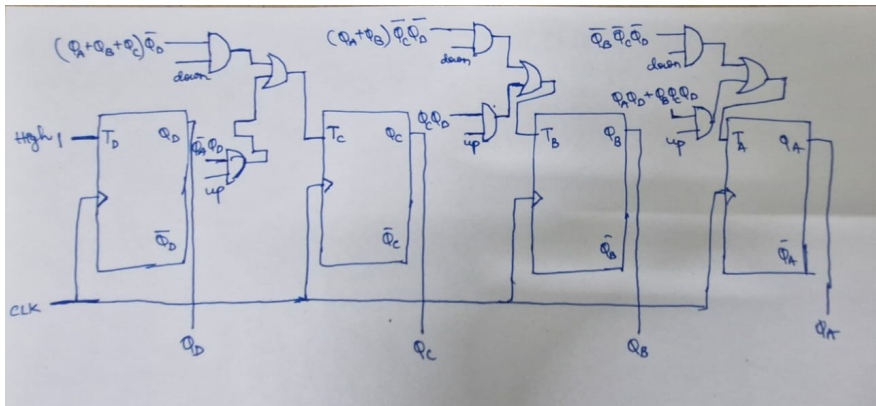
5.1 One's Digit Up Down Counter

Connect the following cascaded counter as in the diagram




- Take 2 pins from the arduino to control up down buttons
- Connect each up down pin as an input to an and gate and the other input as its respective logic
- Give the outputs of each and gate to an or gate and then to each J and K
- Doing this we can control what logic to be performed
- Connect Q_A , Q_B , Q_C , Q_D to the respected 7 segment displays 7447 decoder inputs A B C D

 
Below are some diagrams of the working of a one's digit up down counter, based on the above diagram



After pressing the up button twice

 

 After pressing the down button four times



5.2 Ten's Digit Up Down Counter

- The connections logic remains the same as the one's digit we need to change the clock signal inputs so that it works together as a two digit number
- When the one's digit is at 9 and after pressing up button the ten's digit should increment by 1
- When the one's digit is at 0 and after pressing the down button the ten's digit should decrement by 1
- We implement this logic by changing the ten's digit clock input to the following
- Connect Q_A , Q_B , Q_C , Q_D to the respected 7 segment displays 7447 decoder inputs A B C D

if up logic is to be implemented


$$CLK = Q_3$$

else if down logic is to be implemented


$$CLK = \overline{Q_3}$$

The following logic can be achieved by using AND and OR gates


5.3 Working 0-99-0 Up Down Counter

 

After pressing down button once

 


After pressing up button twice

 

 5.4 Complete Circuit Diagram

- We make 2 independent 0-9 up counters and cascade down logic to that circuit using and and or gates
- We used 2 buttons to for up and down
- Then we connect the clock signal of ten's digit given above logic so that it works together as a 0-99 up down counter

Below is the breadboard connections figure



6 CLK Signal Generation

To control the counting of the one's digit manually, a push button is connected to the Arduino. Each time the button is pressed, the Arduino generates a clock signal and sends it to the T flip-flops. This pulse acts like a clock tick, causing the T flip-flops to toggle and update the count.

- Since push buttons can sometimes cause multiple signals from a single press (known as *bouncing*), the program includes a short delay to ignore such effects. This ensures that one press results in only one proper clock pulse.

Here is the arduino code,

```

1  const int clockPin = 8;
2  const int pulseButton = 6;
3  const int toggleButton = 7;
4  const int pin12 = 12;
5  const int pin13 = 13;
6
7  bool toggleState = true;
8
9  void setup() {
10     pinMode(clockPin, OUTPUT);
11     pinMode(pulseButton, INPUT_PULLUP);
12     pinMode(toggleButton, INPUT_PULLUP);
13     pinMode(pin12, OUTPUT);
14     pinMode(pin13, OUTPUT);
15
16     digitalWrite(pin12, toggleState);

```

```

17 digitalWrite(pin13, !toggleState);
18 }
19
20 void loop() {
21     // Handle toggle button (pin 8)
22     if (digitalRead(toggleButton) == LOW) {
23         delay(50); // Debounce
24         if (digitalRead(toggleButton) == LOW) {
25             toggleState = !toggleState;
26             digitalWrite(pin12, toggleState);
27             digitalWrite(pin13, !toggleState);
28             while (digitalRead(toggleButton) == LOW); // Wait for release
29             delay(50); // Debounce
30         }
31     }
32
33     // Handle clock pulse button (pin 7)
34     if (digitalRead(pulseButton) == LOW) {
35         delay(50); // Debounce
36         if (digitalRead(pulseButton) == LOW) {
37             digitalWrite(clockPin, HIGH);
38             delay(100); // Clock pulse duration
39             digitalWrite(clockPin, LOW);
40             while (digitalRead(pulseButton) == LOW); // Wait for release
41             delay(50); // Debounce
42         }
43     }
44 }


```

The above code functions as follows

- Initializes clockPin (9) as output for generating clock pulses.
- Sets pulseButton (6) and toggleButton (7) as input with internal pull-up resistors.
- pin12 (12) and pin13 (13) are outputs to show the state of toggleState.
- toggleState starts as true, so pin12 = HIGH, pin13 = LOW.
- When toggleButton (pin 7) is pressed:
 - Debounces with delay.
 - If still pressed, toggles toggleState.
 - Updates pin12 and pin13 accordingly: one HIGH, the other LOW.
 - Waits until button is released before continuing.
- When pulseButton (pin 6) is pressed:
 - Debounces with delay.
 - If still pressed, generates a HIGH pulse on clockPin for 100 ms.
 - Then sets clockPin LOW.
 - Waits until button is released before continuing.
- Used for manual control of clock signal and toggling a binary output state.
- Debouncing ensures one response per button press.
- Useful in digital logic testing or manual step-through applications.

7 Problems Faced - Hardware

 - Some IC's were not working properly, which was lately realized
- Forgot to give VCC and GND to the gates sometimes
- Breadboard, wiring issues. Faulty Breadboards and jumper cables
- Push Button debouncing issue



भारतीय प्रौद्योगिकी संस्थान हैदराबाद
Indian Institute of Technology Hyderabad