

Bode Plot of Magnitude and Phase Response for Cascaded RC Low-Pass Filters



Indian Institute of Technology
Hyderabad

Lab Assignment : 03

EE1200: Electrical Circuits Lab

Harshil Rathan Y
Y Akhilesh

EE24BTECH11064
EE24BTECH11066

भारतीय प्रौद्योगिकी संस्थान हैदराबाद
Indian Institute of Technology Hyderabad

Contents

1	Experiment Objectives	2
2	Thoery : Bode Plot	2
2.1	Magnitude Plot	3
2.2	Phase Plot	3
3	Components Used	3
4	Procedure	4
5	1-Stage	4
5.1	Circuit Diagram	4
5.2	Mathematical Analysis for Bode Plot	5
5.2.1	Magnitude Plot	5
5.2.2	Phase plot	5
5.3	Observations and Calculations	6
5.4	Plotting Bode Plot	8
6	2-Stage	8
6.1	Circuit Diagram	8
6.2	Mathematical Analysis for Bode Plot	9
6.2.1	Magnitude Plot	9
6.2.2	Phase plot	9
6.3	Observations and Calculations	10
6.4	Plotting Bode Plot	12
7	3-Stage	13
7.1	Circuit Diagram	13
7.2	Mathematical Analysis for Bode Plot	13
7.2.1	Magnitude Plot for Three-Stage RC Circuit	13
7.2.2	Phase plot	14
7.3	Observations and Calculations	14
7.4	Plotting Bode Plot	16

1 Experiment Objectives

- To analyze the frequency response of 1-stage, 2-stage, and 3-stage RC low-pass filters by measuring the magnitude and phase response.
- To plot the Bode plots (magnitude and phase) and compare the experimental results with theoretical predictions.
- To Compare Single-Stage and Multi-Stage Filters and analyze how the frequency response changes when multiple RC stages are cascaded.

2 Theory : Bode Plot

- An RC circuit consists of a resistor (R) and Capacitor (C) in series or parallel configurations. These circuits are fundamental in signal processing, especially for filtering applications.
- The Bode plot is a graphical representation of a system's frequency response, showing how the gain and phase of the output signal change with frequency.

RC Low-Pass Filter

- A 1-stage RC filter consists of a single of a resistor (R) and a capacitor (C) connected in series, with the output taken across the capacitor.
- The transfer function for a 1-stage RC low pass filter is given by

$$H(s) = \frac{1}{1 + sRC}$$

where $s = j\omega$

Cascading RC Low-Pass Filter

- When multiple RC sections are cascaded, the overall transfer function becomes the product of individual transfer functions.

For n identical RC stages

$$H_n(s) = \left(\frac{1}{1 + sRC} \right)^n$$

Transfer function for a 2-Stage RC Low-pass filter

$$H(s) = \frac{1}{(1 + sRC)^2}$$

Transfer function for a 3 Stage RC Low-Pass filter

$$H(s) = \frac{1}{(1 + sRC)^3}$$

- Each additional stage increases the roll-off rate by -20 dB/decade, making the overall filter steeper. The phase response is also affected, introducing additional phase lag.

Cutoff Frequency

It is given by

$$f_c = \frac{1}{2\pi RC}$$

- At this frequency, the output voltage drops to $\frac{1}{\sqrt{2}}$ (about 70.7) of the input voltage, corresponding to a -3 dB gain reduction in the Bode plot. Beyond f_c , the filter attenuates signals at a rate of -20 dB/decade for a single stage.

2.1 Magnitude Plot

It is a Gain vs Frequency plot

The Magnitude response in dB is given by

$$|H(j\omega)|_{\text{dB}} = 20 \log_{10} \left(\frac{1}{\sqrt{1 + (\omega RC)^2}} \right)$$

- At Low frequencies ($\omega \ll \omega_c$) The gain is approximately 0
- At cut-off frequency ($\omega = \omega_c$) The gain drops to -3 dB
- At High Frequencies ($\omega \gg \omega_c$) The gain decreases at a slope of -20 dB/decade

2.2 Phase Plot

It is a Phase Shift vs Frequency plot, given by

$$\angle H(j\omega) = -\tan^{-1}(\omega RC)$$

- At Low frequencies ($\omega \ll \omega_c$) The phase shift is approximately 0°
- At cut-off frequency ($\omega = \omega_c$) The phase shift is approx -45°
- At High Frequencies ($\omega \gg \omega_c$) The phase shift approaches -90°

3 Components Used

Function Generator

- Supplies and Generates an adjustable periodic waveforms (e.g., sine waves) to evaluate the frequency response.
- Enables variation of signal frequency to observe magnitude and phase response.

Oscilloscope

- Displays the voltage waveform over time, enabling real-time signal analysis.
- Measures amplitude attenuation and phase shift across different filter stages.
- Provides frequency-domain analysis when used in conjunction with Fast Fourier Transform (FFT) functions.

Resistors

- Control the charging and discharging time of capacitors.
- Influence the cutoff frequency .
- Affect the overall attenuation and phase characteristics of the filter.

In this experiment, we used $10k\Omega$ resistors

Capacitors

- Store and release charge, controlling signal attenuation at different frequencies.
- Influence the phase shift of the output signal relative to the input.
- Play a key role in defining the filter's behavior when cascaded.

In this experiment, we used $220\mu F$ capacitors.

Breadboard

- Facilitates quick circuit assembly and reconfiguration.
- Simplifies testing of different cascading configurations.

4 Procedure


- Choose resistor (R) and capacitor (C) values to achieve a desired cutoff frequency and calculate the cutoff frequency $f_c = \frac{1}{2\pi RC}$
- Connect all the components on the breadboard and build 1-Stage, 2-Stage, 3-Stage RC Low-Pass filters
- Connect the function generator to the input of the filter.
- Connect the oscilloscope to both the input and output of the filter.
- Set the function generator to produce a sinusoidal waveform with amplitude 5V
- Start with the cutoff frequency and gradually increase the frequency in multiples of that cutoff freq.
- At each frequency, measure the output voltage using the oscilloscope.
- Calculate and record the gain for every V_{out} and plot the required bode plot

$$Gain(dB) = 20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$

- Use the oscilloscope to measure the phase difference between the input and output signals.
- At each frequency, note the phase shift and plot the required bode plot

5 1-Stage

5.1 Circuit Diagram

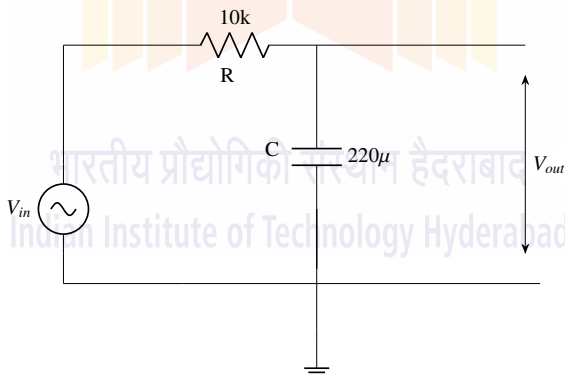

5.2 Mathematical Analysis for Bode Plot

5.2.1 Magnitude Plot

The Transfer function is given by

$$H(s) = \frac{V_{out}}{V_{in}} \quad H(s) = \frac{\frac{1}{j\omega C}}{1 + \frac{1}{j\omega C}}$$

$$H(s) = \frac{1}{1 + j\omega RC}$$

The magnitude of the transfer function:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

For our given values of R and C ,

$$RC = 2.2$$

Thus magnitude simplifies to:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (4.84)\omega^2}}$$

The gain in decibels is given by,

$$\text{Gain} = 20 \log_{10} |H(j\omega)| = -20 \log_{10} \sqrt{1 + 4.84\omega^2}$$

For different values of ω :

- When $\omega \ll a$:

$$\text{Gain} \approx 0$$

- When $\omega = a$:

$$\text{Gain} \approx -20 \log_{10}(\sqrt{2}) \approx -10 \log_{10} 2 = -3.010299.....$$

- When $\omega \gg a$:

$$\text{Gain} \approx -10 \log_{10}(2.2\omega)$$

5.2.2 Phase plot

The transfer function is given by

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

The phase is given by

$$\angle H(j\omega) = \tan^{-1} \left(\frac{\text{Imaginary part}}{\text{Real part}} \right) = \tan^{-1}(-\omega RC)$$

On substituting $R = 10k\Omega$ and $C = 220\mu F$

$$RC = 2.2$$

$$\angle H(j\omega) = \tan^{-1}(-2.2\omega)$$

- When $\omega \ll a$: Using small angle approximations $\tan^{-1}(x) = x$

$$\angle H(j\omega) \approx -2.2\omega$$

- When $\omega = a$: The phase is approximately -45°

$$\angle H(j\omega) = \tan^{-1}(-1) = -45^\circ$$

- When $\omega \gg a$: The phase reaches -90°

$$\angle H(j\omega) \approx \tan^{-1}(-\infty) = -90^\circ$$

Where $a = \frac{1}{RC}$, the cutoff value of ω


The phase changes from 0° to 90° as ω increases, it reaches -45° at $\omega = \frac{1}{RC}$

$$\text{Phase} = \begin{cases} 0^\circ, & \omega < 0.1a \\ \text{Slope} = -45^\circ/\text{dec} & \omega \approx a \\ -90^\circ, & \omega > 10a \end{cases}$$

5.3 Observations and Calculations

Let us now verify the values obtained on the oscilloscope with the ones obtained on simulation

- **Frequency** = $0.0723Hz$

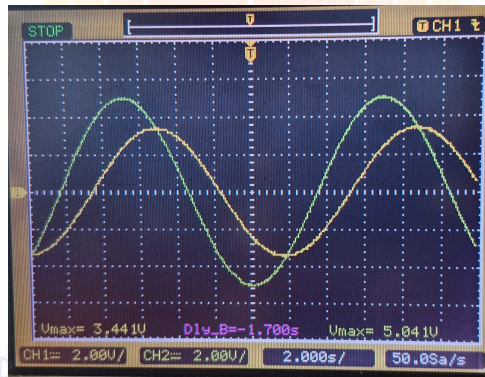


- **Gain** = -3.316
- **Phase** = $-44.98 \approx -45$
- **Frequency** = $7.23Hz$





- Gain = -37.921
- Phase = -89.42

- Frequency = 723Hz

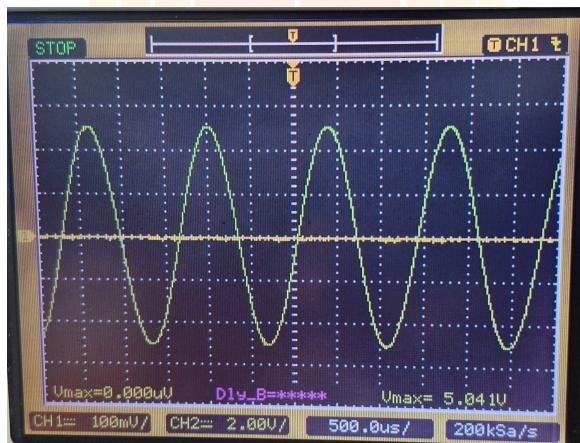


- Gain ≈ -45
- Phase = -89.99 ≈ -90

5.4 Plotting Bode Plot

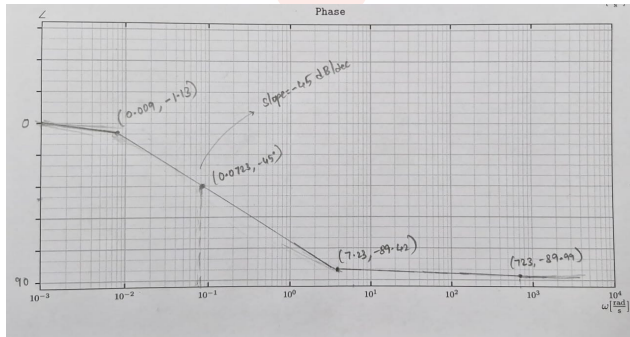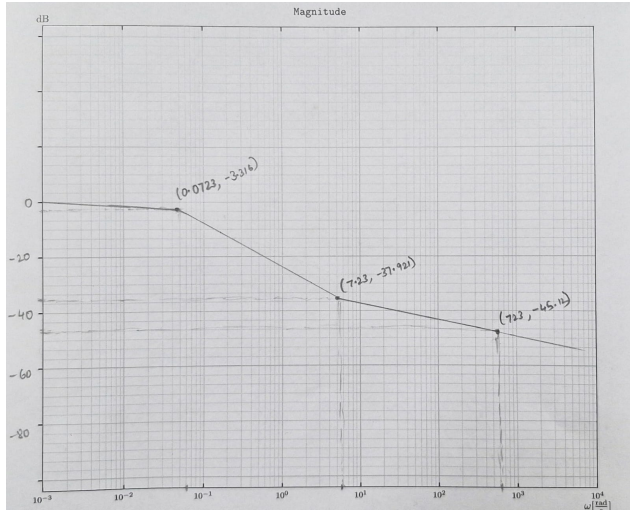

6 2-Stage

6.1 Circuit Diagram

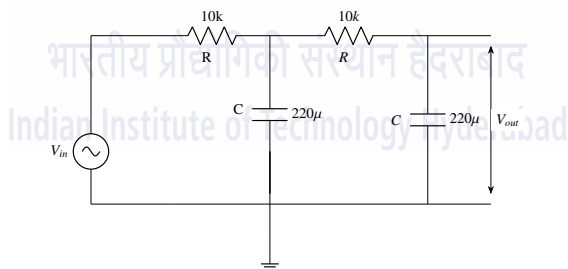

6.2 Mathematical Analysis for Bode Plot

6.2.1 Magnitude Plot

The Transfer function for a two-stage RC circuit is given by:

$$H(j\omega) = \frac{1}{(1 + j\omega RC)^2}$$

The magnitude of the transfer function is:

$$|H(j\omega)| = \frac{1}{1 + (\omega RC)^2}$$

For the given values of R and C :

$$RC = 2.2$$

Thus, the magnitude simplifies to:

$$|H(j\omega)| = \frac{1}{1 + 4.84\omega^2}$$

The gain in decibels is given by:

$$\text{Gain} = 20 \log_{10}(|H(j\omega)|) = -20 \log_{10}(1 + 4.84\omega^2)$$

For different values of ω :

- When $\omega \ll a$:

$$\text{Gain} \approx 0$$

- When $\omega = a$ (cutoff frequency):

$$\text{Gain} \approx -20 \log_{10} 2 \approx -6.0205 \text{ dB}$$

- When $\omega \gg a$ (high frequency):

$$\text{Gain} \approx -20 \times 2 \log_{10}(2.2\omega) \approx -40 \log(2.2\omega)$$

6.2.2 Phase plot

For a two-stage RC circuit, the transfer function is given by

$$H(j\omega) = \frac{1}{(1 + j\omega RC)^2}$$

The phase response is

$$\angle H(j\omega) = \tan^{-1}(-\omega RC) + \tan^{-1}(-\omega RC)$$

$$\angle H(j\omega) = 2 \tan^{-1}(-\omega RC)$$

On substituting $R = 10k\Omega$ and $C = 220\mu F$

$$RC = 2.2$$

$$\angle H(j\omega) = 2 \tan^{-1}(-2.2\omega)$$

- When $\omega \ll a$: Using small angle approximations $\tan^{-1}(x) = x$

$$\angle H(j\omega) \approx 2(-2.2\omega) \approx -4.4\omega$$

- When $\omega = a$: The phase is approximately -90°

$$\angle H(j\omega) = 2 \tan^{-1}(-1) = 2(-45^\circ) = 2(-45^\circ) = -90^\circ$$

- When $\omega \gg a$: The phase reaches -180°

$$\angle H(j\omega) \approx 2 \tan^{-1}(-\infty) = 2(-90^\circ) = -180^\circ$$

Where $a = \frac{1}{RC}$, the cutoff value of ω


Thus, for a two-stage RC filter, the phase shifts from 0° to -180° , reaching -90° at $\omega = \frac{1}{RC}$ with a steeper slope of $-90^\circ/\text{decade}$ compared to the $-45^\circ/\text{decade}$ slope of a single-stage RC filter.

$$\text{Phase} = \begin{cases} 0^\circ, & \omega < 0.1a \\ \text{Slope} = -90^\circ \text{ dB/dec}, & \omega \approx a \\ -180^\circ, & \omega > 10a \end{cases}$$

6.3 Observations and Calculations

Let us now verify the values obtained on the oscilloscope with the ones obtained on simulation

- **Frequency = 0.0723Hz**

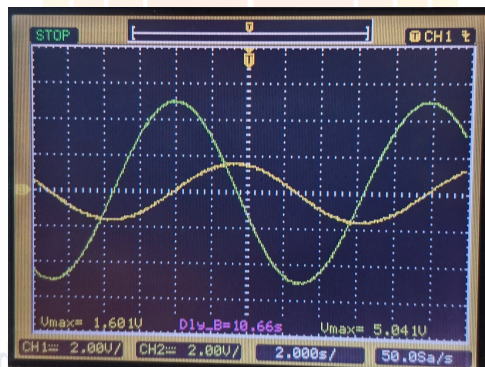


- Gain = -9.967
- Phase = -89.96
- **Frequency = 7.23Hz**





- Gain = -69.963
- Phase = -178.84

- Frequency = 723Hz

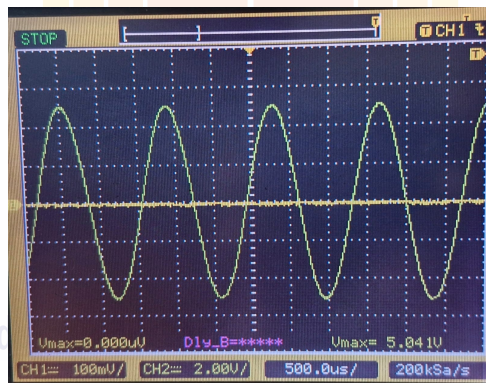


- Gain ≈ -128.062
- Phase = -178.98

6.4 Plotting Bode Plot

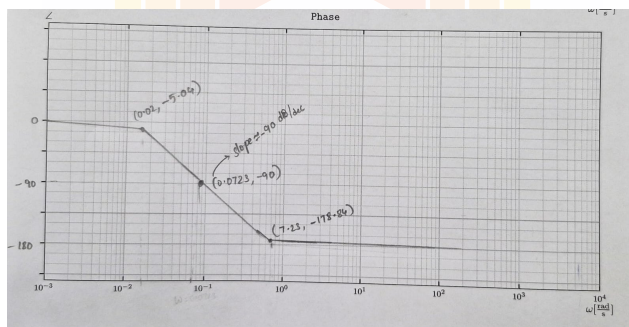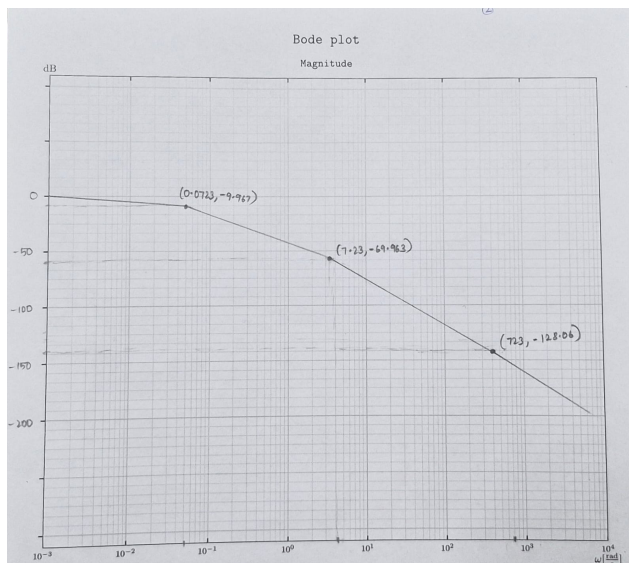

7 3-Stage

7.1 Circuit Diagram

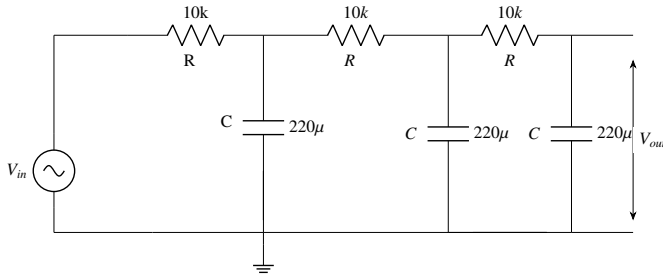

7.2 Mathematical Analysis for Bode Plot

7.2.1 Magnitude Plot for Three-Stage RC Circuit

The Transfer function for a three-stage RC circuit is given by:

$$H(j\omega) = \frac{1}{(1 + j\omega RC)^3}$$

The magnitude of the transfer function is:

$$|H(j\omega)| = \frac{1}{(1 + (\omega RC)^2)^{3/2}}$$

For the given values of R and C :

$$RC = 2.2$$

Thus, the magnitude simplifies to:

$$|H(j\omega)| = \frac{1}{(1 + 4.84\omega^2)^{3/2}}$$

The gain in decibels is given by:

$$\text{Gain} = 20 \log_{10} (|H(j\omega)|) = -30 \log_{10} (1 + 4.84\omega^2)$$

For different values of ω :

- When $\omega \ll a$ (low frequency):

$$\text{Gain} \approx 0$$

In this case, the gain is very close to 0 dB because the frequency is much lower than the cutoff frequency.

- When $\omega = a$ (cutoff frequency):

$$\text{Gain} \approx -30 \log_{10} 2 \approx -30 \times 0.3010 = -9.03 \text{ dB}$$

- When $\omega \gg a$ (high frequency):

$$\text{Gain} \approx -60 \log_{10} (2.2\omega)$$

This reflects the roll-off of the third-order filter with a slope of -60 dB/decade.

7.2.2 Phase plot

For a three-stage RC circuit, the transfer function is given by

$$H(j\omega) = \frac{1}{(1 + j\omega RC)^3}$$

The phase response is

$$\angle H(j\omega) = \tan^{-1}(-\omega RC) + \tan^{-1}(-\omega RC) + \tan^{-1}(-\omega RC)$$

$$\angle H(j\omega) = 3 \tan^{-1}(-\omega RC)$$

On substituting $R = 10k\Omega$ and $C = 220\mu F$

$$RC = 2.2$$

$$\angle H(j\omega) = 3 \tan^{-1}(-2.2\omega)$$

- When $\omega \ll a$: Using small angle approximations $\tan^{-1}(x) = x$

$$\angle H(j\omega) \approx 3(-2.2\omega) \approx -6.6\omega$$

- When $\omega = a$: The phase is approximately -135°

$$\angle H(j\omega) = 3 \tan^{-1}(-1) = 3(-45^\circ) = -135^\circ$$

- When $\omega \gg a$: The phase reaches -180°

$$\angle H(j\omega) \approx 3 \tan^{-1}(-\infty) = 3(-90^\circ) = -270^\circ$$

Where $a = \frac{1}{RC}$, the cutoff value of ω

Thus, for a three-stage RC filter, the phase shifts from 0° to -270° , reaching -135° at $\omega = \frac{1}{RC}$ with a steeper slope of $-135^\circ/\text{decade}$ compared to the $-90^\circ/\text{decade}$ slope of a two-stage RC filter.

$$\text{Phase} = \begin{cases} 0^\circ, & \omega < 0.1a \\ \text{Slope} = -135^\circ \text{ dB/dec}, & \omega \approx a \\ -270^\circ, & \omega > 10a \end{cases}$$

7.3 Observations and Calculations


Let us now verify the values obtained on the oscilloscope with the ones obtained on simulation

- **Frequency** = 0.0723Hz




- Gain = -15.98
- Phase = -134.94

- Frequency = 7.23Hz

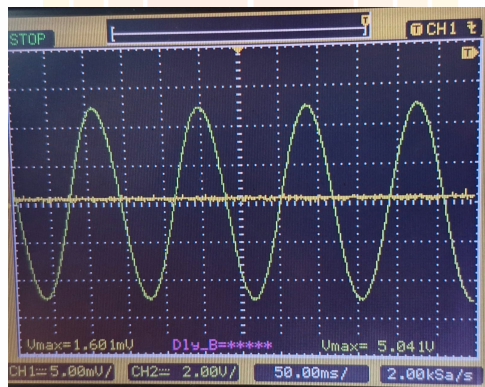


- Gain = -69.96
- Phase = -268.26


- Frequency = 723Hz

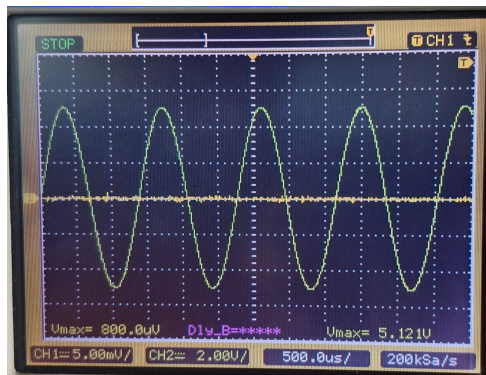

- Gain = -192.094
- Phase = -269.97

7.4 Plotting Bode Plot

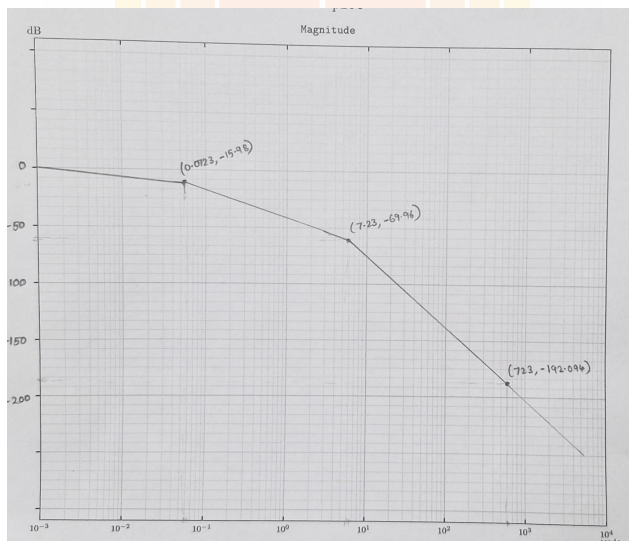

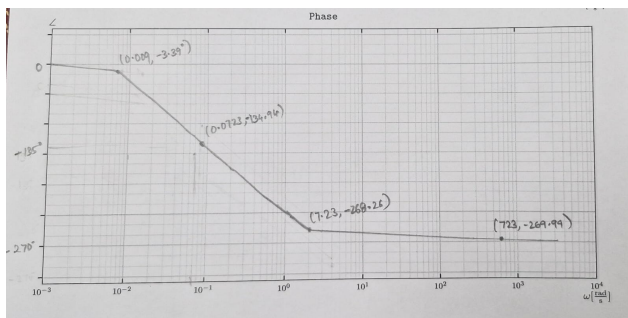

भारतीय प्रौद्योगिकी संस्थान हैदराबाद
Indian Institute of Technology Hyderabad