

# Op-Amp Applications

- 1. Custom Weighted Summing & Difference Amplifier
- 2. Op-Amp Integrator
- 3. Precision Rectifier (Super Diode)



Indian Institute of Technology  
Hyderabad

## Lab Assignment : 05

EE1200: Electrical Circuits Lab

Harshil Rathan Y  
Y Akhilesh

EE24BTECH11064  
EE24BTECH11066


भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

## Contents

<b>1</b>	<b>LM358</b>	<b>2</b>
<b>2</b>	<b>Weighted Summing &amp; Difference Amplifier</b>	<b>2</b>
2.1	Components Required . . . . .	2
2.2	Circuit Diagram . . . . .	3
2.3	Procedure . . . . .	3
2.4	Observation . . . . .	5
<b>3</b>	<b>Op-Amp Integrator</b>	<b>6</b>
3.1	Components Required . . . . .	6
3.2	Circuit Diagram . . . . .	6
3.3	Theory . . . . .	7
3.4	Observation . . . . .	8
<b>4</b>	<b>Precision Rectifier</b>	<b>9</b>
4.1	Components Required . . . . .	9
4.2	Circuit Diagram . . . . .	10
4.3	Circuit set-up . . . . .	10
4.4	Theory . . . . .	10
4.5	Observations . . . . .	12
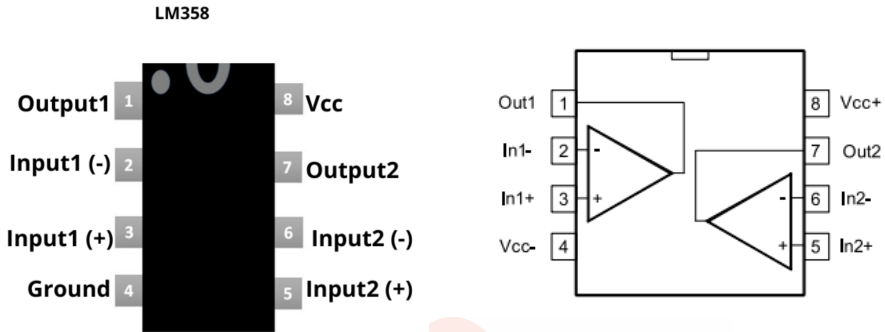
## 1 LM358

The LM358 is a low-power, dual-operational amplifier (op-amp) IC designed for general-purpose applications. It consists of two independent, high-gain op-amps that operate from a single power supply.



The pin-out diagram for LM358 is give above

### Features and Uses


- **Dual Op-Amp in a Single Package:** Provides two independent op-amps, saving space and cost.
- **Low Power Consumption:** Each amplifier draws only  $500\mu A$ , making it ideal for low-power designs.
- **Works with a wide voltage range (3V to 32V),** unlike many op-amps that require dual supplies.
- **Used to amplify signals from sensors** like temperature sensors, strain gauges, and pressure sensors.
- **Generates triangular and square waveforms** when used in oscillator circuits.
- **Used in low-pass, high-pass, and band-pass filters** in audio and signal processing circuits.

## 2 Weighted Summing & Difference Amplifier


### 2.1 Components Required

- Op-Amp IC - LM358
- Resistors -
- Function Generator
- Oscilloscope
- DC Power Supply

## 2.2 Circuit Diagram

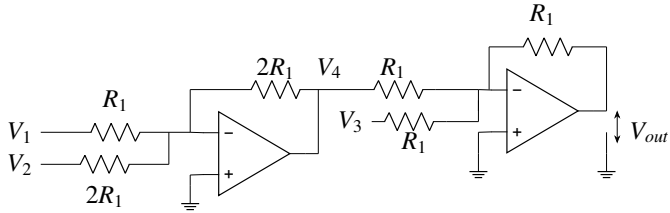

### Breadboard Connection

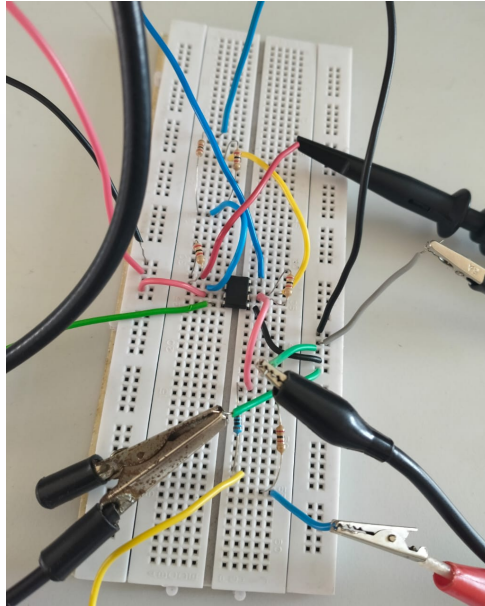

## 2.3 Procedure

### Derivation of the Weighted Summing and Difference Amplifier Output

#### Circuit Design

The circuit consists of two operational amplifier (op-amp) stages:

#### 1) First op-amp (Inverting Summing Amplifier)


- Takes three input voltages:  $V_1$ ,  $V_2$ , and  $V_3$ .
- Performs weighted summation using properly chosen resistors.
- Produces an intermediate output  $V_{out1}$ .

#### 2) Second op-amp (Inverting Amplifier)

- Takes  $V_{out1}$  as input and inverts it.
- This inversion helps achieve the required final output  $V_{out}$ .

For general case,

### Derivation of Output Equation

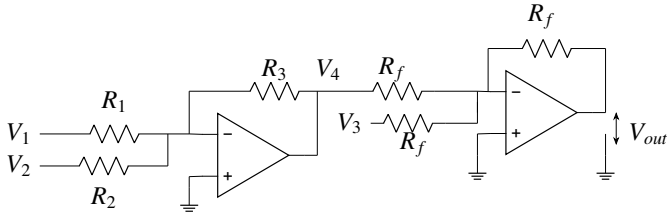

Applying Kirchhoff's Current Law (KCL) at the inverting input

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{V_{out1}}{R_f} \quad (2.1)$$

Multiplying by  $R_f$ :

$$V_{out1} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) \quad (2.2)$$

Choosing resistors:

$$\begin{aligned} \frac{R_f}{R_1} &= 2 \Rightarrow R_f = 2R_1 \\ \frac{R_f}{R_2} &= 1 \Rightarrow R_f = R_2 \\ \frac{R_f}{R_3} &= -1 \Rightarrow R_f = -R_3 \end{aligned}$$

Thus, we obtain:

$$V_{out1} = -(2V_1 + V_2 - V_3) \quad (2.3)$$

The second stage is an inverting amplifier with gain  $-1$ :

$$V_{out} = -V_{out1} \quad (2.4)$$

Substituting:

$$V_{out} = 2V_1 + V_2 - V_3 \quad (2.5)$$

This confirms that the circuit correctly implements the desired function.

### Special Case for the Second Function

If  $V_2 = 0$ , then:


$$V_{out} = 2V_1 - V_3 \quad (2.6)$$

which matches the second required function.

Thus, the circuit fully satisfies the given mathematical functions.

## 2.4 Observation


on Oscilloscope,

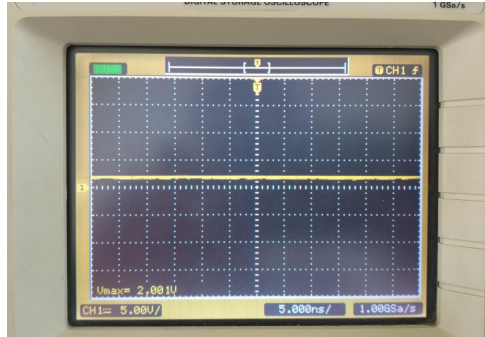

for the input power source,



input values in function generator,

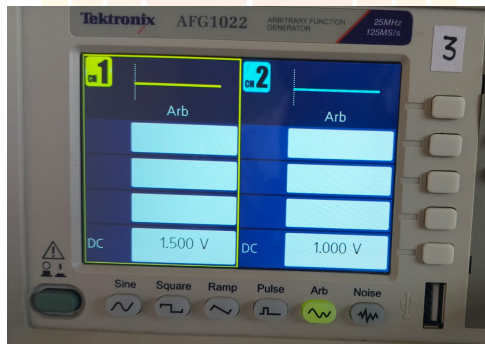

## Validation

checking the output voltage,

$$2V_1 + V_2 - V_3$$

Here,

- $V_3$  is the voltage reading in the power source i.e 2V

$$V_1 = 1.5V$$

$$V_2 = 1V$$

Therefore the calculated output voltage,

$$2(1.5) + 1 - 2 = 2V$$

and it matches to the experimental output i.e 2.001V


- The circuit correctly implements the weighted sum and difference as required.
- By selecting appropriate resistor values, the desired coefficients in the equation are achieved.
- The two-stage design ensures correct polarity of the final output.


### 3 Op-Amp Integrator

#### 3.1 Components Required

- Op-Amp IC - LM358
- Resistor -  $10k\Omega$
- Capacitor -  $100\mu F$
- Function Generator
- Oscilloscope
- DC Power Supply

#### 3.2 Circuit Diagram

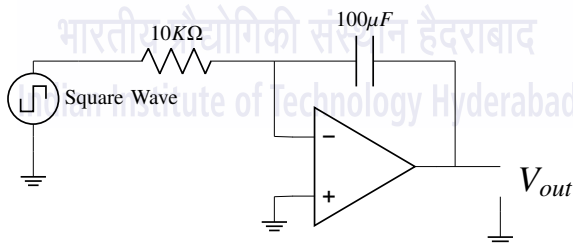

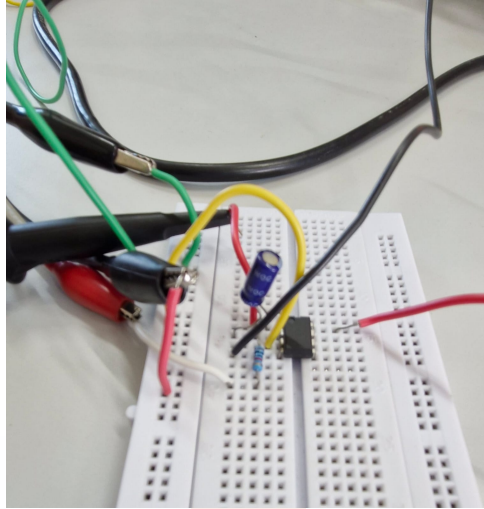

### 3.3 Theory

An Op-Amp integrator is a circuit that performs mathematical integration of the input signal. The output signal is proportional to the integral of the input signal, which is given by

It consists of

- A resistor in series with the input signal
- A capacitor in the feedback loop

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$

For  $R = 10k\Omega$  and  $C = 100\mu F$

$$V_{out} = -1 \int V_{in} dt$$

This means that the output voltage is the negative integral of the input voltage.

### Applications

- It converts a square wave to triangular waveform - Waveform Generation
- Low pass filtering effect

#### 1) Power Connections:

- Connect +12 V from the power supply to the  $V_{cc+}$  pin of the op-amp. (Pin 8)
- Connect 0 V to the  $V_{cc-}$  pin of the op-amp. (Pin 4)
- Connect the ground (GND) of the power supply to the circuit ground.

#### 2) Resistor and Capacitor Connections:



- Connect one end of the resistor ( $R$ ) to the input voltage source (square wave from function generator).
- Connect the other end of the resistor ( $R$ ) to the inverting input ( $-$ ) of the op-amp.
- Connect the capacitor ( $C$ ) between the output of the op-amp and the inverting input ( $-$ ) of the op-amp .
- Connect the non-inverting input ( $+$ ) of the op-amp to ground.

### 3) Function Generator:

- Set up the function generator to produce a square wave signal (e.g., 1 kHz frequency, 5V peak-to-peak).
- Connect the function generator output to the resistor ( $R$ ).

### 4) Oscilloscope Connection:

- **Channel 2 (CH2)** of the oscilloscope: Connect to the input square wave signal.
- **Channel 1 (CH1)** of the oscilloscope: Connect to the output of the op-amp.

**Note:** The ground clips of both **CH1** and **CH2** probes must be connected to the circuit ground (**GND**) to ensure proper reference and avoid floating signals.

### Analysis

For  $R = 10k\Omega$  and  $C = 100\mu F$

$$V_{out} = -1 \int V_{in} dt$$

CH2 is the input signal with


- Frequency = 1Hz
- Amplitude = 2.0V

CH1 is the measure output signal across the ends of the  $1k\Omega$  Resistor

भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad
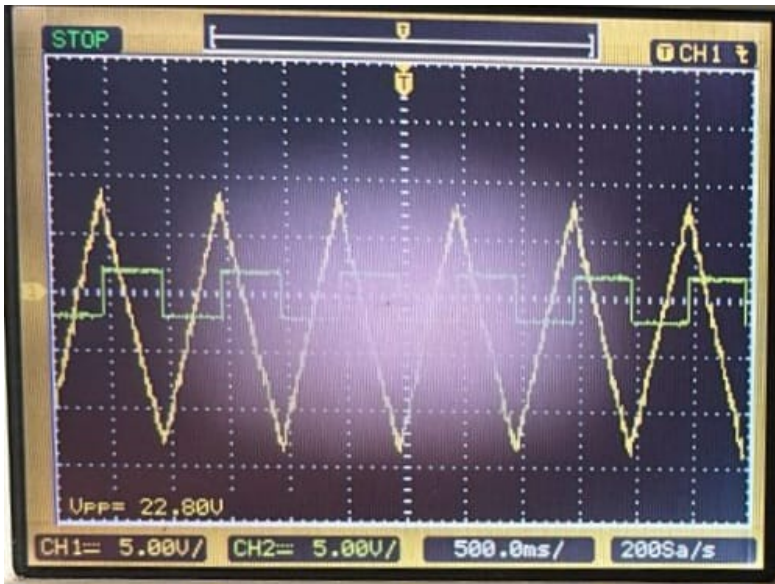
### 3.4 Observation

We observe that the square wave input is converted into triangular wave output.




## 4 Precision Rectifier


### 4.1 Components Required

- Op-Amp IC - LM358
- Diode - 1N4148
- Resistors
- AC Signal Generator
- Oscilloscope

## 4.2 Circuit Diagram

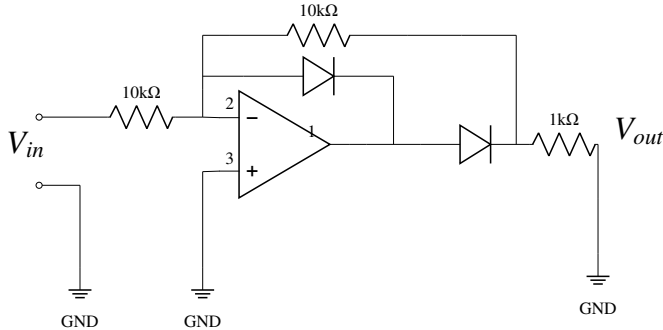

## Breadboard Connections

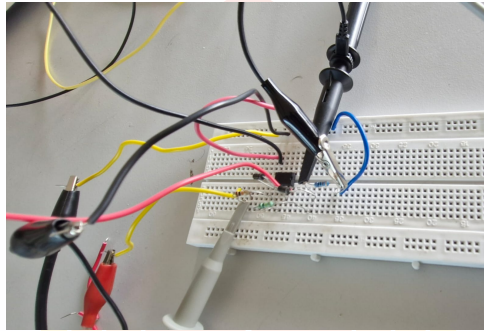

## 4.3 Circuit set-up

- Connect one end of the resistor( $10k\Omega$ ) to pin 2 of LM358 and the other end to the  $V_{in}$
- Connect the pin 3 of LM358 to GND
- Connect a resistor( $10k\Omega$ ) between pin 2 and pin 1 of LM358
- Connect 2 diodes in series between pin 2 and pin 1
- Connect a resistor ( $1k\Omega$ ) from pin 1 to GND and measure the  $V_{out}$

## 4.4 Theory

A precision rectifier, also called a super diode, is an op-amp-based rectifier circuit that can rectify signals with very small voltages, overcoming the 0.7V diode forward voltage drop of conventional rectifiers.

### Half-Wave Rectifier

- The circuit connections are shown in the diagram above
- A half-wave precision rectifier allows only the positive half of an AC signal to pass while blocking the negative half.

## Operation

- During the positive half-cycle, the op-amp output drives the diode into conduction, allowing the signal to pass.
- During the negative half-cycle, the diode blocks conduction, preventing the negative signal from reaching the output.
- Which results in a half wave rectifier

## Analysis

For the input sine wave

$$V_{in}(t) = A \sin(2\pi f)$$

where

- $f = 80\text{kHz}$
- $A = 1$

for  $V_{in} > 0$

- The diode conducts, and the output follows the input.

$$V_{out}(t) = V_{in}(t) = \sin(2\pi 80000)t$$

for  $V_{in} < 0$

- The diode blocks the signal, and the output is zero.



$$V_{out}(t) = 0$$

The waveform is given by

$$V_{out}(t) = \begin{cases} \sin(2\pi(80,000)t), & \text{if } V_{in} > 0 \\ 0, & \text{if } V_{in} < 0 \end{cases}$$

the following waveform can be observed below

## 4.5 Observations

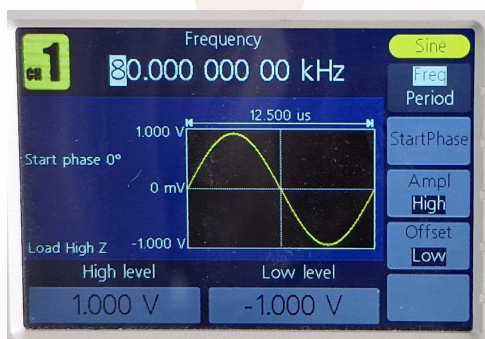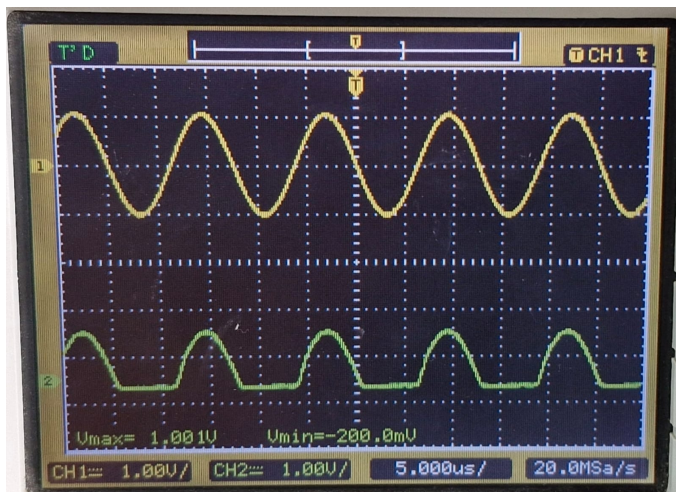

भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad